

Integration of the General Network Theorem in ADE and ADE XL

Toward a Deeper Insight Into Circuit Behavior

Jochen Verbrugghe
Bart Moeneclaey

jochen.verbrugghe@intec.ugent.be

bart.moeneclaey@intec.ugent.be

Integration of the General Network Theorem in ADE and ADE XL

General Network Theorem

Integration in ADE (XL)

Application example

General Network Theorem

Decomposition of transfer function in simpler parts:
lower-level transfer functions, *useful for design*

Using test signal injection and nulling techniques

$$H = H_{\infty} \frac{1 + \frac{1}{T_n}}{1 + \frac{1}{T}} = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

Using multiple injections T , T_n and H_0 can be further factored

Ref: R. D. Middlebrook 2006, IEEE Microwave Magazine

General Network Theorem: N-EET and CT

Injection points determine decomposition and interpretation

GNT morphs into three interpretations

N-Extra Element Theorem (N-EET)

N injections

$$H = H_{\infty} \frac{1 + \frac{1}{T_n}}{1 + \frac{1}{T}}$$

Extra Elements absent
Effect of Extra Elements

Chain Theorem (CT)

single V or I injection

$$H = H_{\infty} \frac{1}{1 + \frac{1}{T}}$$

Buffered gain
Loading effect of second stage

General Network Theorem: GFT

Injection points determine decomposition and interpretation

GNT morphs into three interpretations

General Feedback Theorem (GFT)

V and I injection

$$H = H_{\infty} \frac{1 + \frac{1}{T_n}}{1 + \frac{1}{T}}$$
$$= H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

- 'Ideal' transfer function, infinite loop gain
- Loop gain
- Null loop gain
- Direct feedthrough, zero loop gain

Lower-level TF factorization
example: loop gain T

$$T = \frac{T_{\text{fwd}}}{1 + T_{\text{rev}}}$$
$$T_{\text{fwd}} = T_{\text{v,fwd}} \parallel T_{\text{i,fwd}}$$
$$T_{\text{rev}} = T_{\text{v,rev}} \parallel T_{\text{i,rev}}$$

Compare to *stb* loop gain T_t

$$T_t = T_{\text{fwd}} + T_{\text{rev}}$$

Integration of the General Network Theorem in ADE and ADE XL

General Network Theorem

Integration in ADE (XL)

Application example

Integration in ADE (XL): motivation

GNT advantages

- General framework

 - Same techniques for different applications, hand calculations

 - Well-known results derive cleanly from GNT

- Results are useful for design

- Divide-and-conquer approach

Integration in Virtuoso



- Application of GNT to real-world designs

 - Deeper insight into complex circuit behavior

- Find out dominant lower-level TFs (a priori)

- Validate hand-analysis results (a posteriori)

Integration in ADE (XL): circuit setup

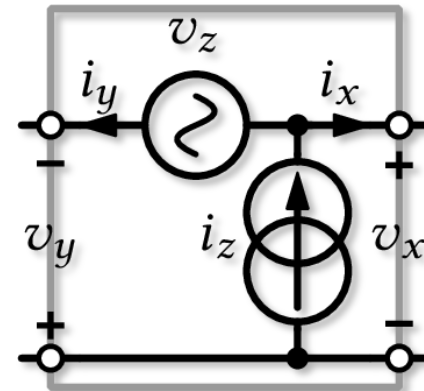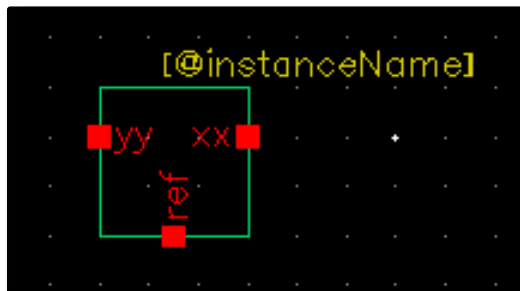

Insert GNT Probes in schematic at appropriate points

Inject small-signal test signals: voltage and/or current

Uninvasive

Does not interfere with other analyses


Layout XL and Calibre LVS tools supported

Integration in ADE (XL): analysis setup



- New analysis 'gnt' in Choosing Analysis...
Same use model as stb, ac, ...
- Familiar options
Sweep variable, sweep range, sweep type
- Source instance, output net or probe
Indicates the transfer function H to decompose
- (Nested) GNT analyses
GNT Probe instance(s)
Analysis type: GFT, N-EET, CT

Integration in ADE (XL): internals

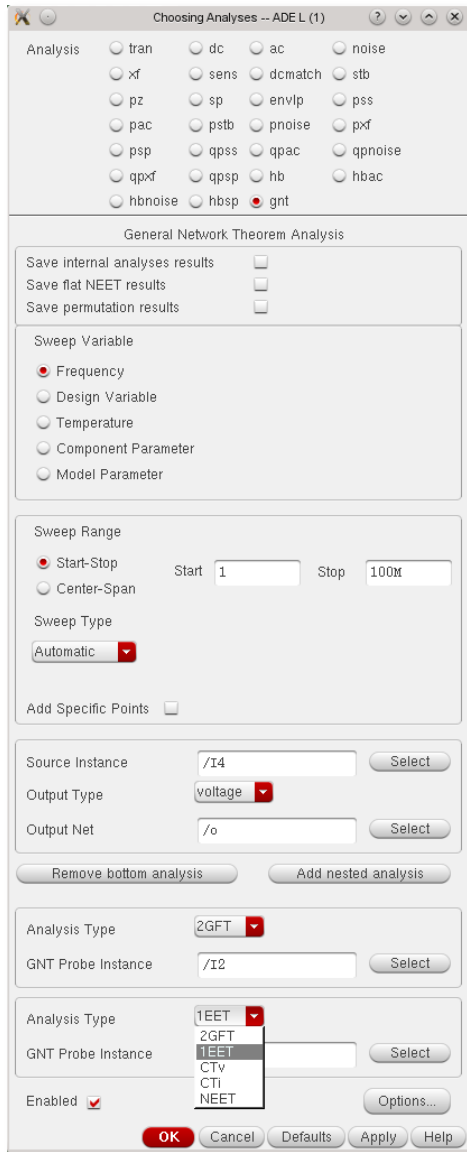

Internally always flat N-EET calculated


Using AC analysis per injection

- Data to be saved optionally

Flat N-EET results

Any possible permutations of nested analyses

Integration in ADE (XL): results

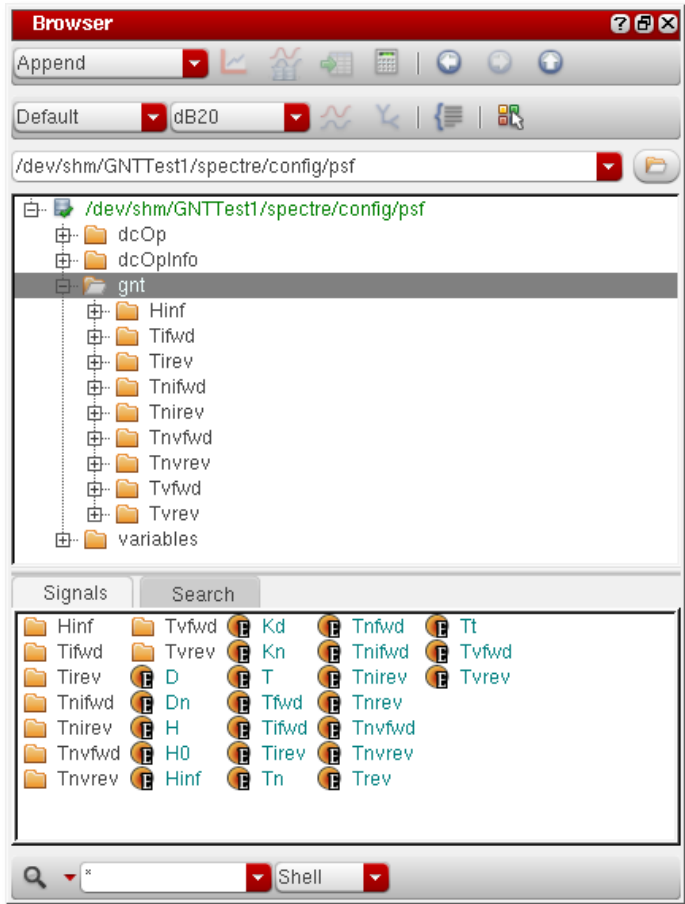


Results included in psf data
Nested results as folders

Accessible in the usual ways
ViVa's Results Browser
getData() SKILL API

GFT Tt identical to *stb* loop gain
Given identical reference nodes

Integration in ADE (XL): ADE support

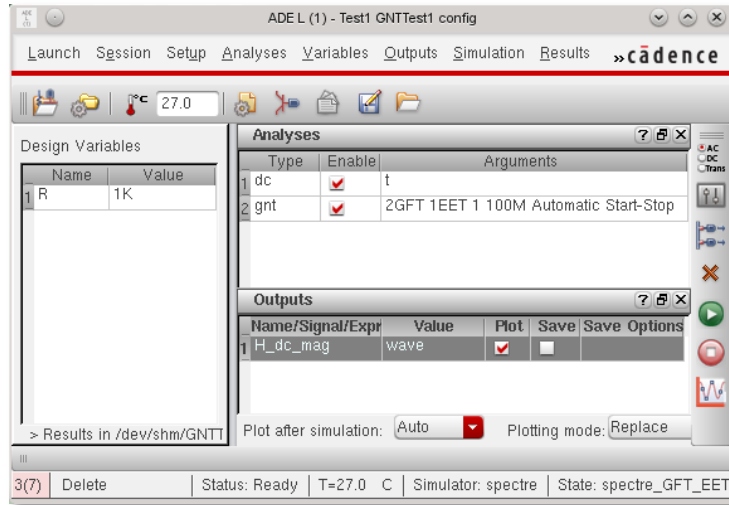

ADE L

Incl. parametric sweep

ADE (G)XL

Corners

Parameters

Monte Carlo sampling


Sensitivity analysis

Optimization

Worst-case corners

...

Tested in IC 6.1.5 and IC 6.1.6

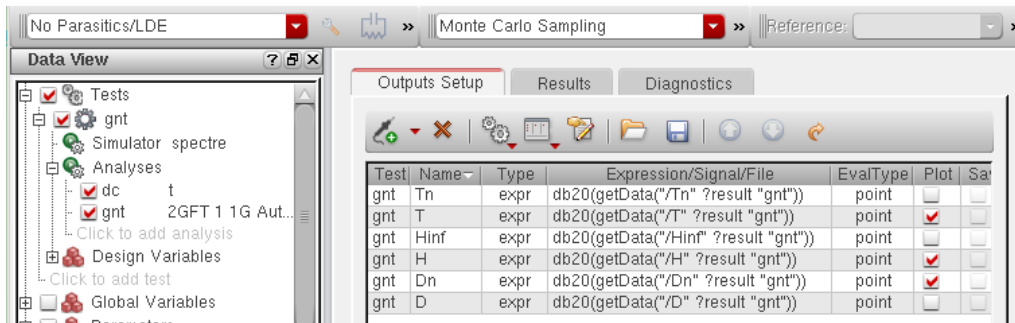

Integration of the General Network Theorem in ADE and ADE XL

General Network Theorem

Integration in ADE (XL)


Application example

Application example: voltage regulator

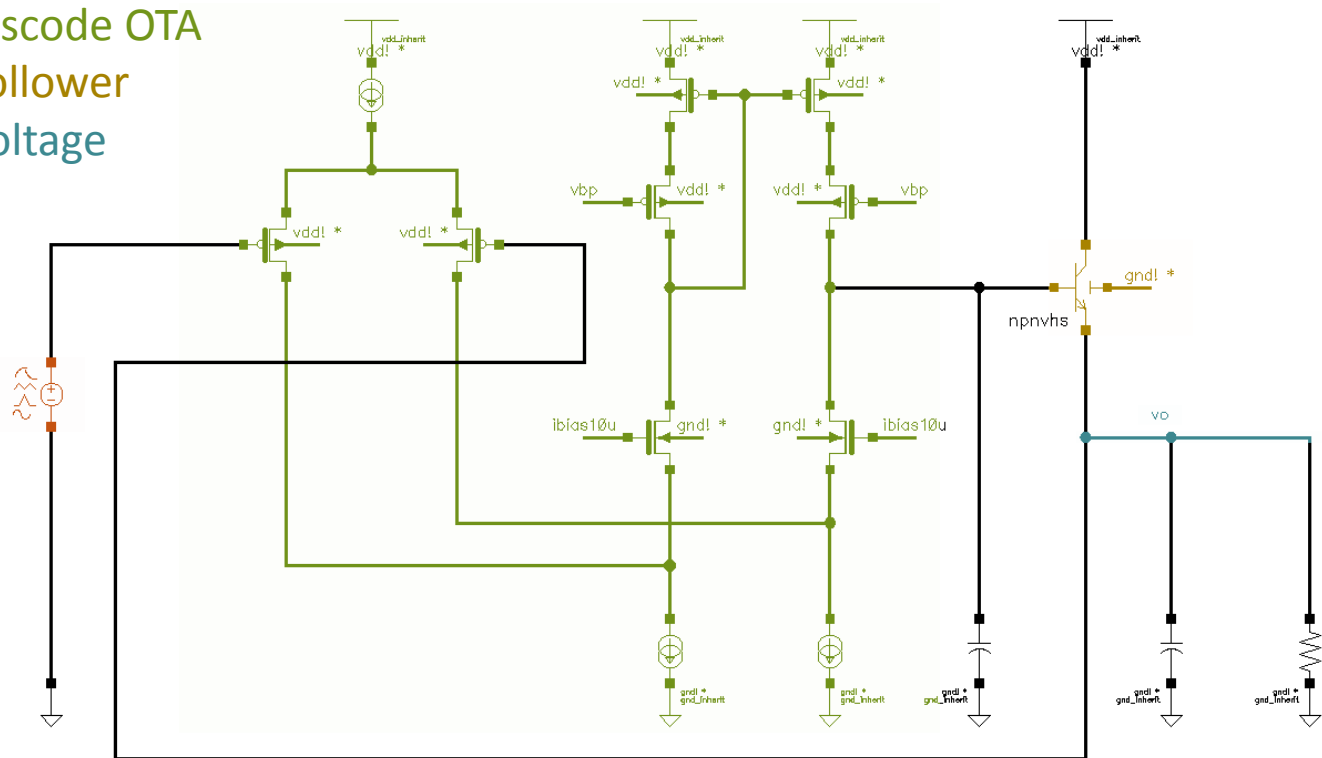Problem

Output voltage inaccurate

- Input voltage source
- Folded cascode OTA
- Emitter follower
- Output voltage



Application example: GFT analysis - setup

Source Instance:


Output Type:

Output Net:

Analysis Type:

GNT Probe Instance:


GFT analysis

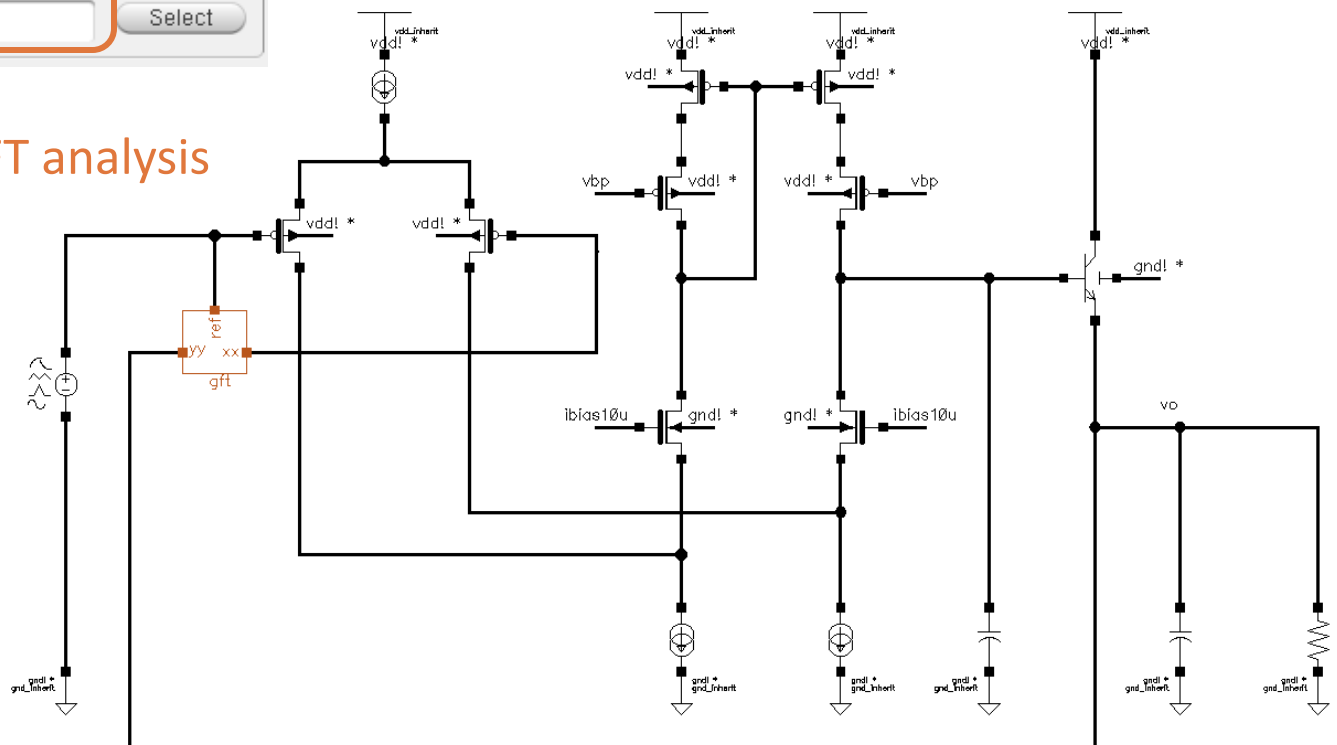

Application example: GFT analysis - results

Problem

Output voltage inaccurate

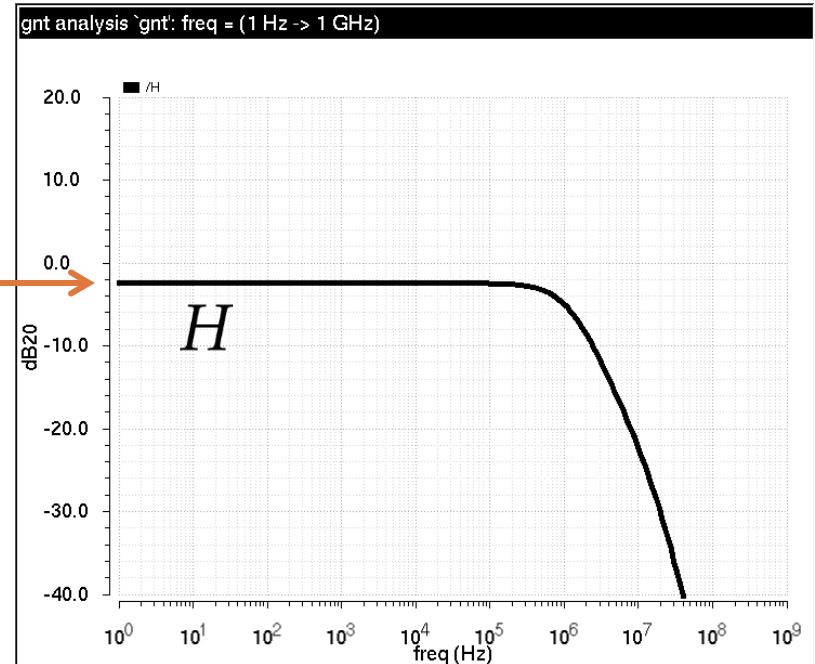

$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$


Application example: GFT analysis - results

Problem

H too low

↳ Output voltage inaccurate
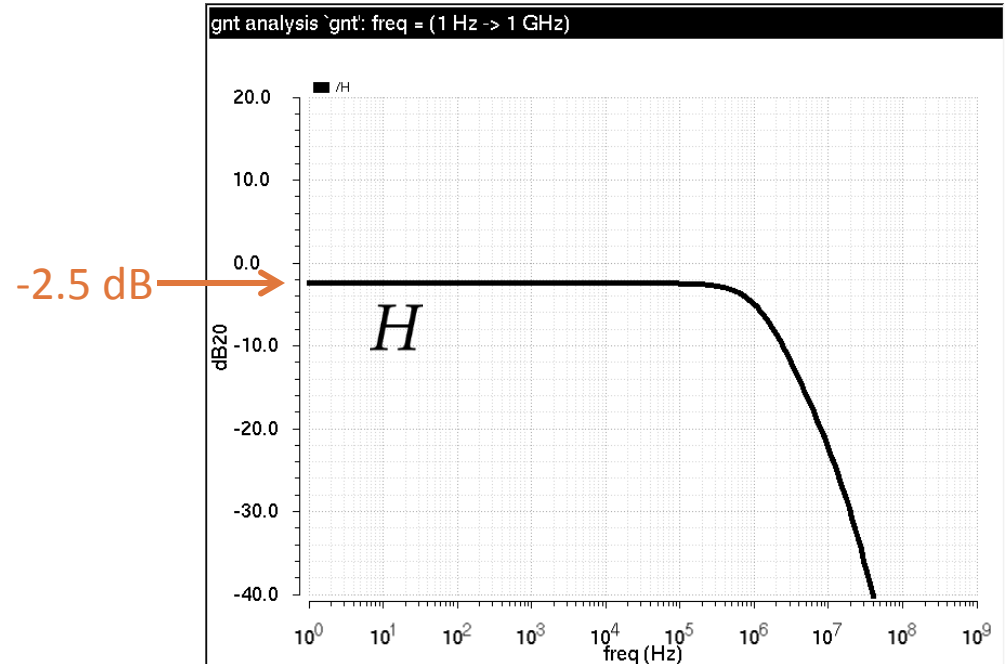
$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$




Application example: GFT analysis - results

Problem

H too low

↳ Output voltage inaccurate
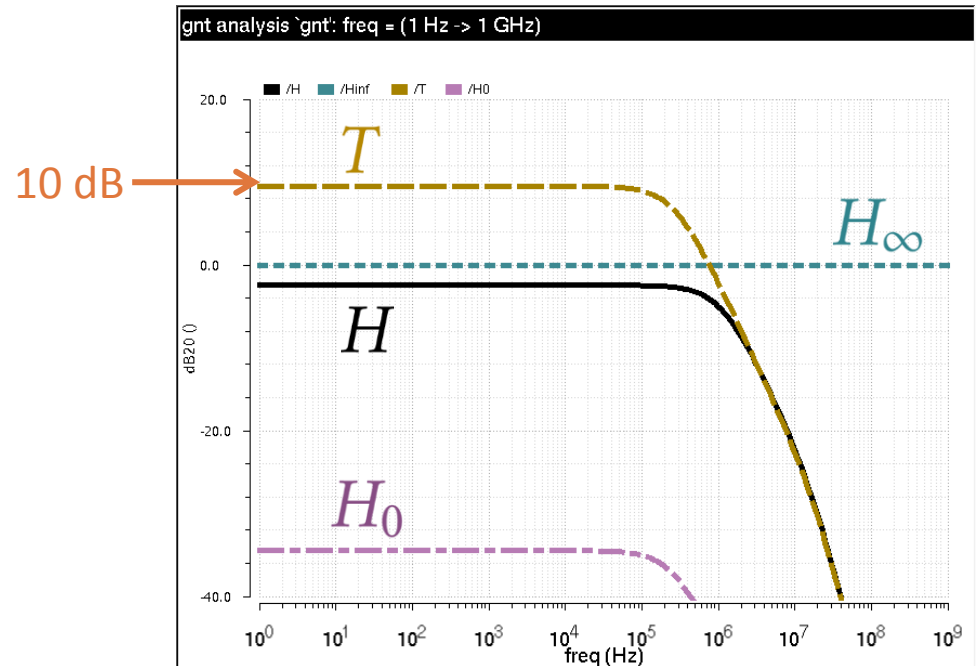
$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$




Application example: GFT analysis - results

Problem


Forward voltage loop gain insufficient
 ↳ H too low
 ↳ Output voltage inaccurate

$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

$$T \approx T_{v,\text{fwd}}$$

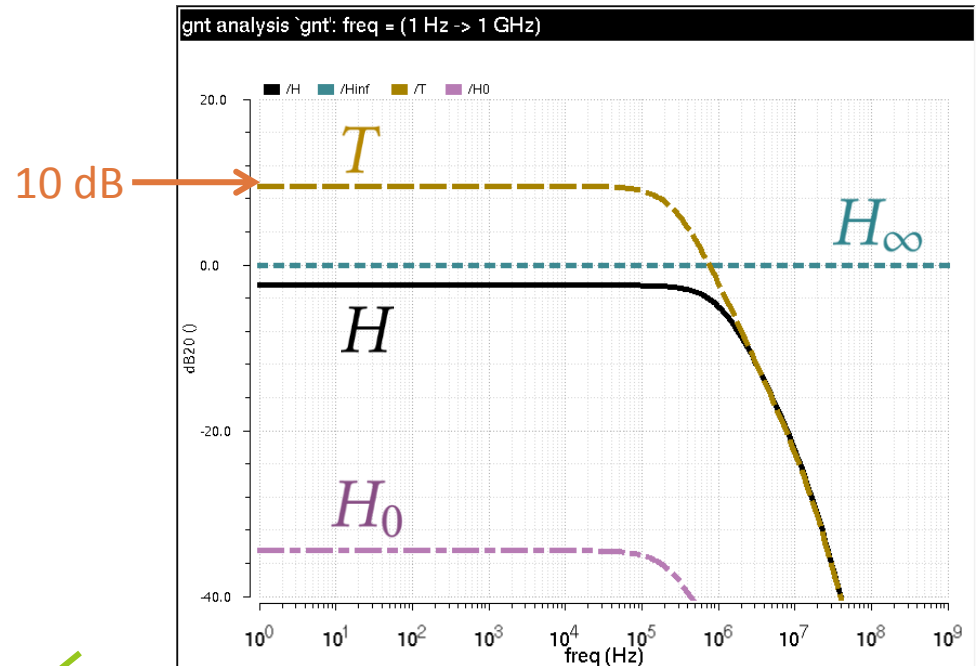

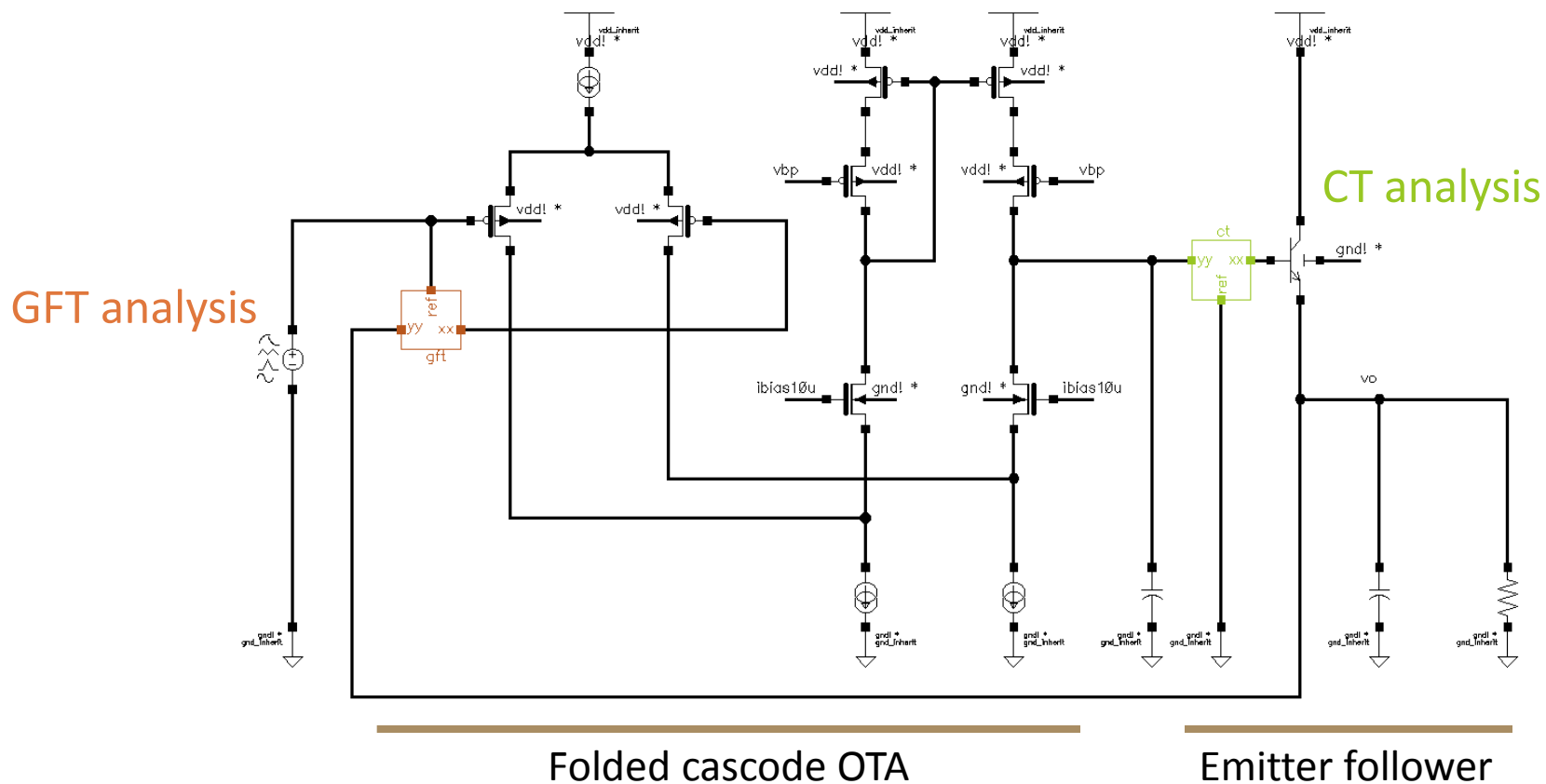Application example: CT analysis nested in GFT analysis - setup



Application example: CT analysis nested in GFT analysis - setup


Remove bottom analysis Add nested analysis

Analysis Type: 2GFT
GNT Probe Instance: /gft Select

Analysis Type: CTv
GNT Probe Instance: /ct Select

GFT analysis

CT analysis

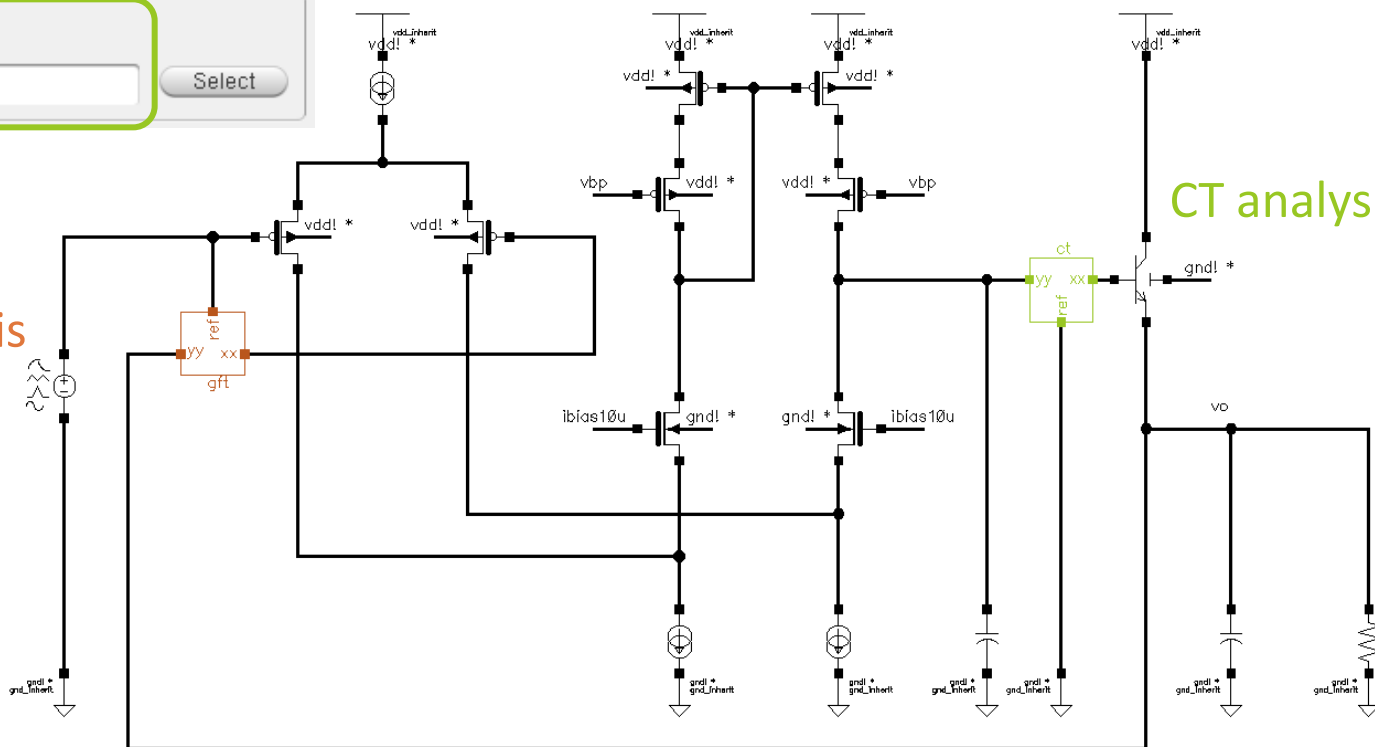

Folded cascode OTA

Emitter follower

Application example: CT analysis nested in GFT analysis - results


Problem

Forward voltage loop gain insufficient

↳ H too low

↳ Output voltage inaccurate
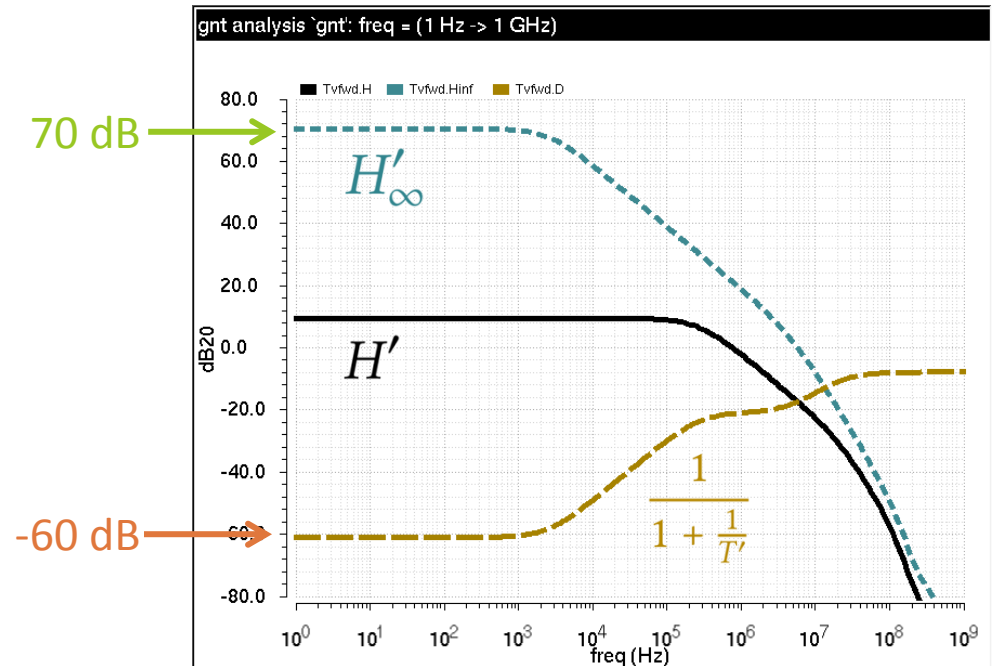
$$T_{v,\text{fwd}} = H'$$
$$H' = H'_{\infty} \frac{1}{1 + \frac{1}{T'}}$$




Application example: CT analysis nested in GFT analysis - results

Problem

Excessive interaction between stages
 ↳ Forward voltage loop gain insufficient
 ↳ H too low
 ↳ Output voltage inaccurate


$$T_{V,\text{fwd}} = H'$$
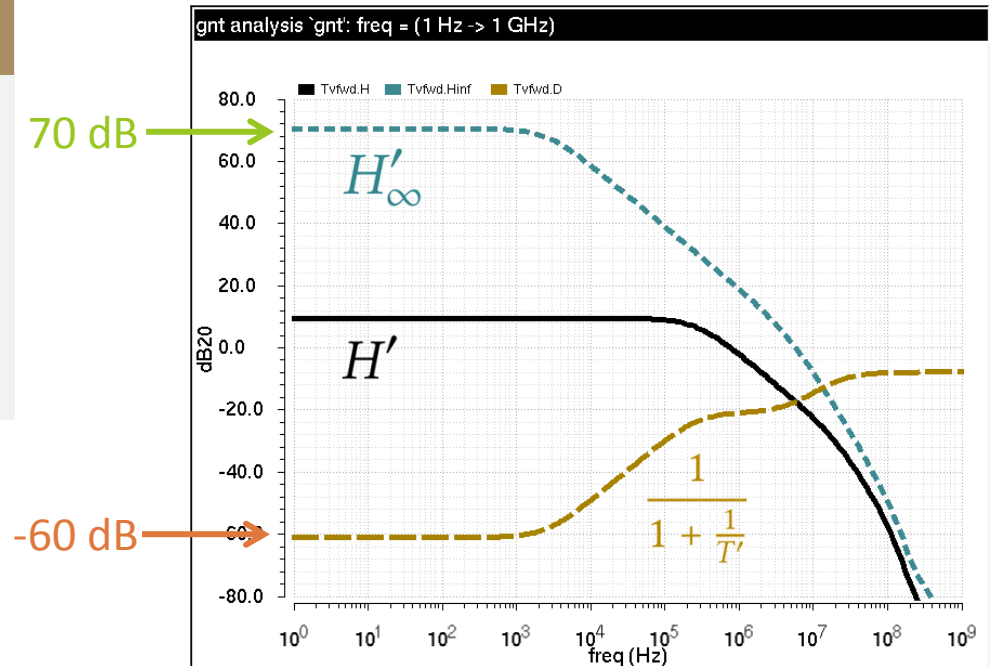
$$H' = H'_\infty \frac{1}{1 + \frac{1}{T'}}$$



Application example: reducing the interaction between stages


Insert a PMOS source follower

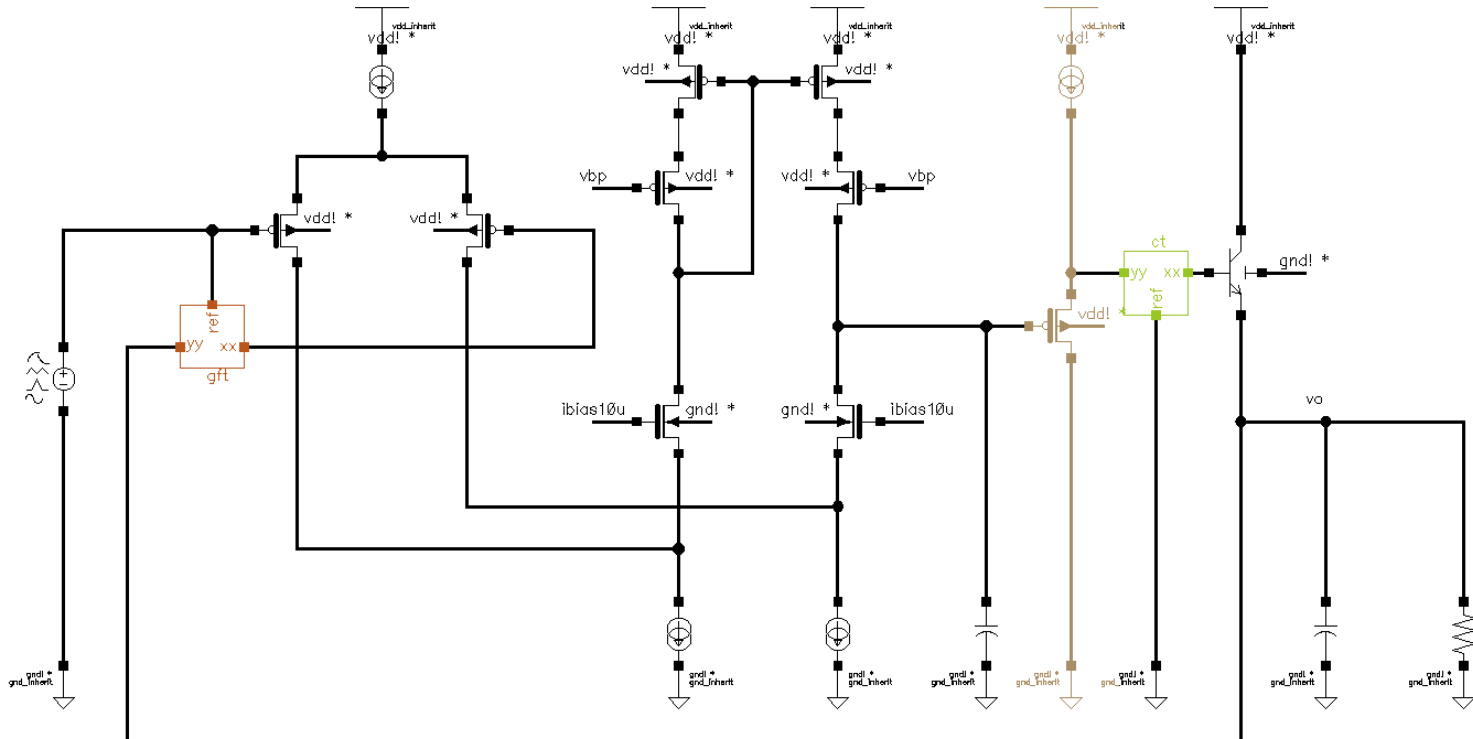

Application example: reducing the interaction between stages - results

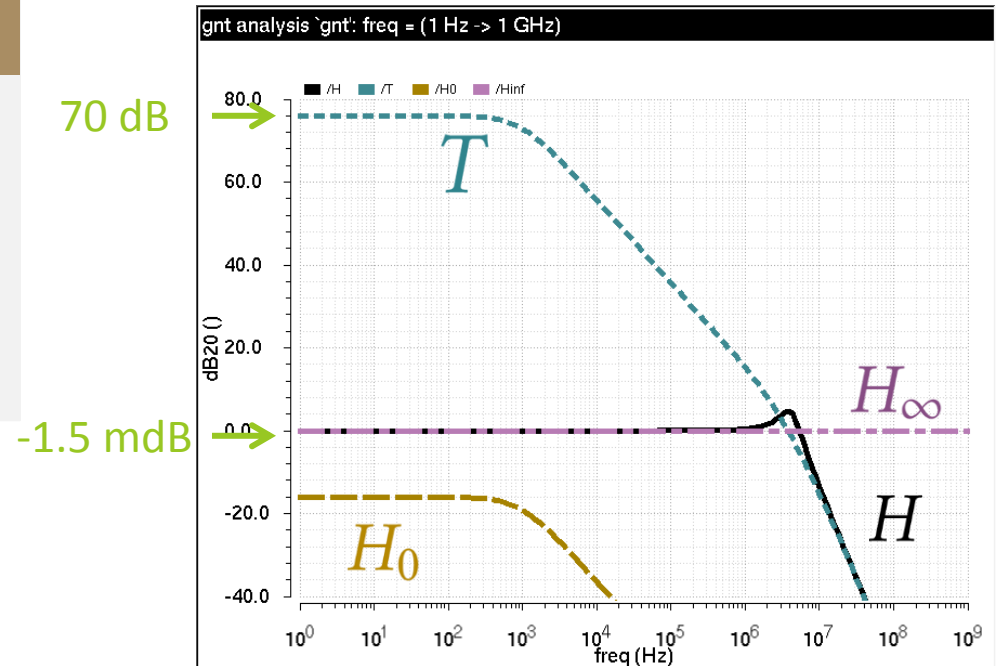Problem


- Excessive interaction between stages
 - ↳ Forward voltage loop gain insufficient
 - ↳ H too low
 - ↳ Output voltage inaccurate



Application example: reducing the interaction between stages - results

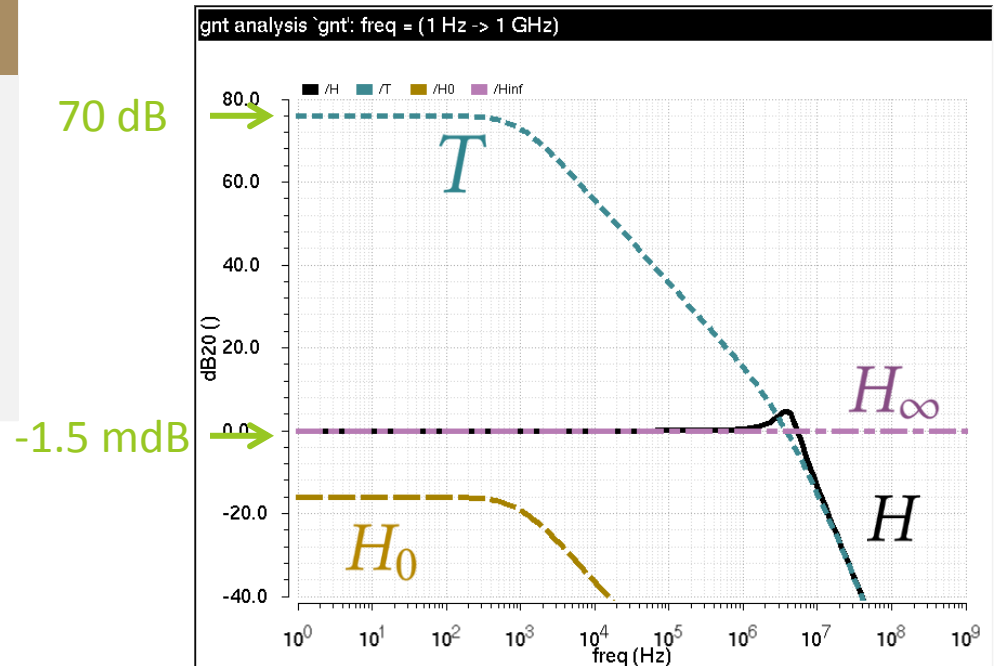Problem


- Excessive interaction between stages
 - ↳ Forward voltage loop gain insufficient
 - ↳ H too low
 - ↳ Output voltage inaccurate



Application example: reducing the interaction between stages - results

Problem

H shows peaking

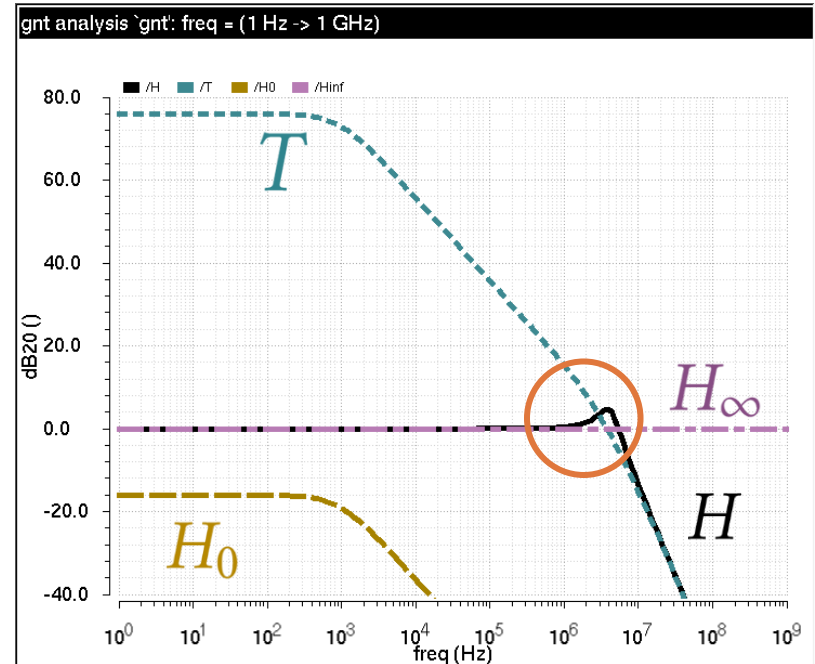


$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

Application example: reducing the interaction between stages - results

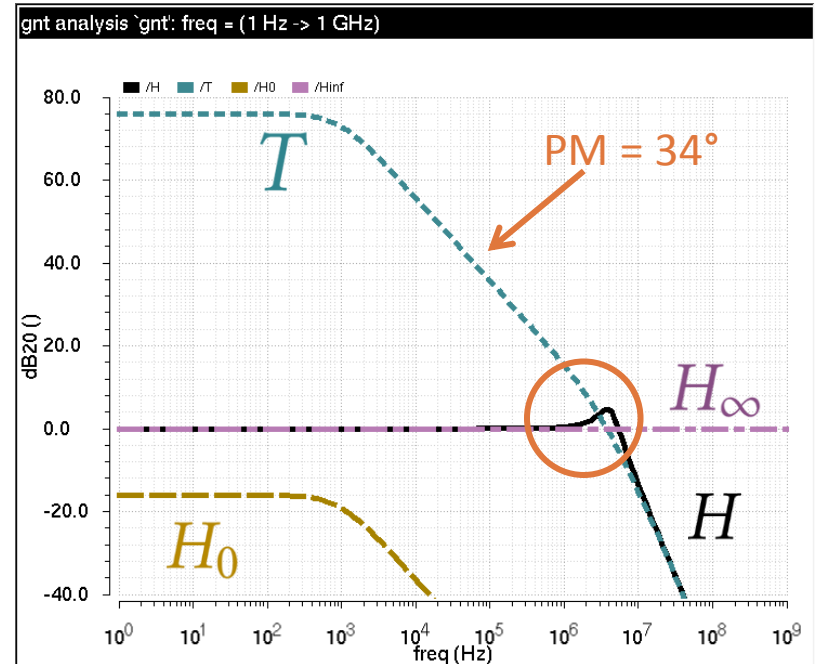Problem

Forward voltage loop gain
insufficient phase margin
↳ H shows peaking



$$H = H_{\infty} \frac{T}{1 + T} + H_0 \frac{1}{1 + T}$$

$$T \approx T_{v,\text{fwd}}$$


Application example: reducing peaking, EET analysis nested in GFT analysis - setup

Remove bottom analysis Add nested analysis

Analysis Type: **2GFT** (selected)
GNT Probe Instance: `/gft` Select

Analysis Type: **NEET** (selected)
GNT Probe Instance: `/eet` Select

GFT analysis

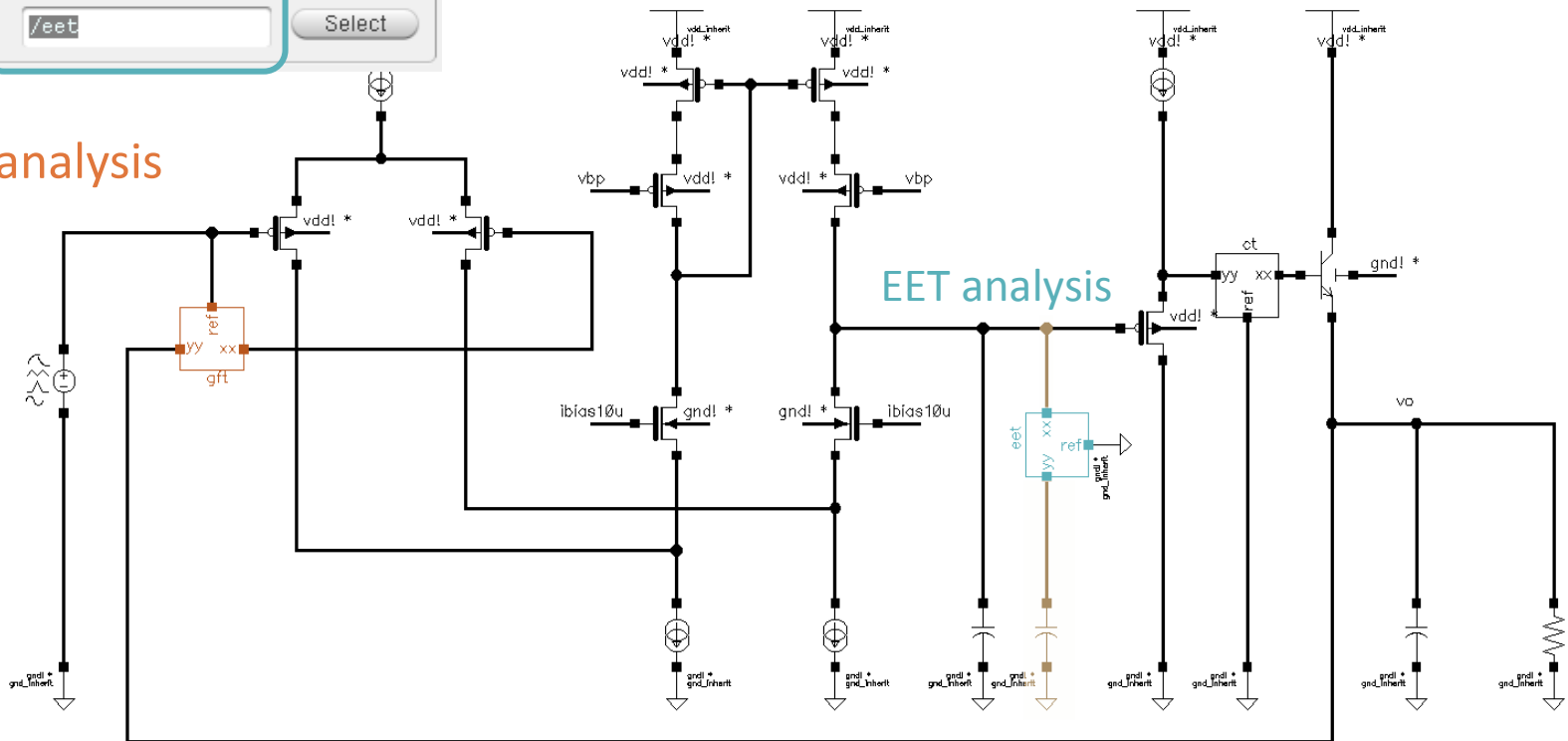

additional capacitance


Application example: reducing peaking, EET analysis nested in GFT analysis - results

Problem

Forward voltage loop gain
insufficient PM
↳ H shows peaking

$$T_{v,\text{fwd}} = H'$$
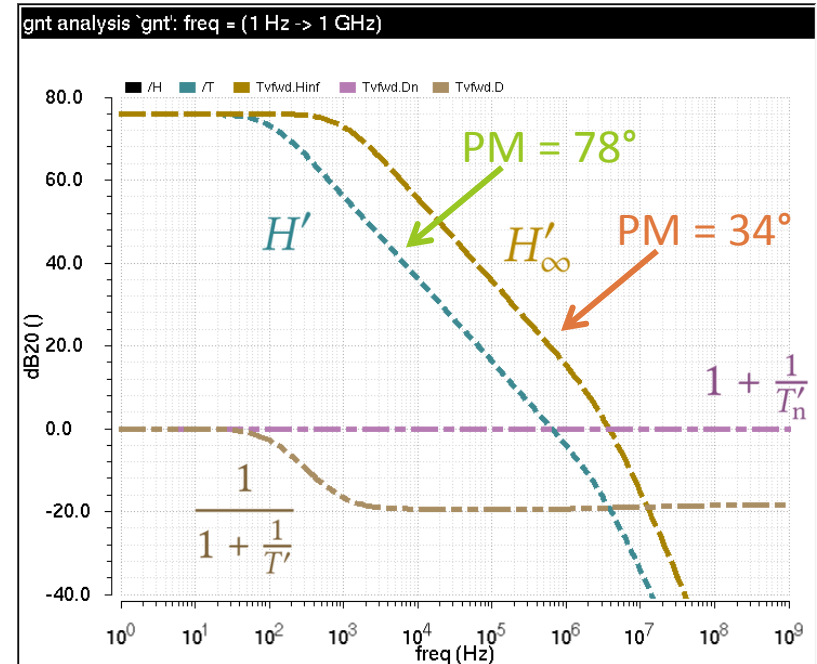
$$H' = H'_\infty \frac{1 + \frac{1}{T'_n}}{1 + \frac{1}{T'}}$$




Application example: reducing peaking, EET analysis nested in GFT analysis - results

Problem

Forward voltage loop gain
insufficient PM
↳ H shows peaking

$$T_{v,\text{fwd}} = H'$$
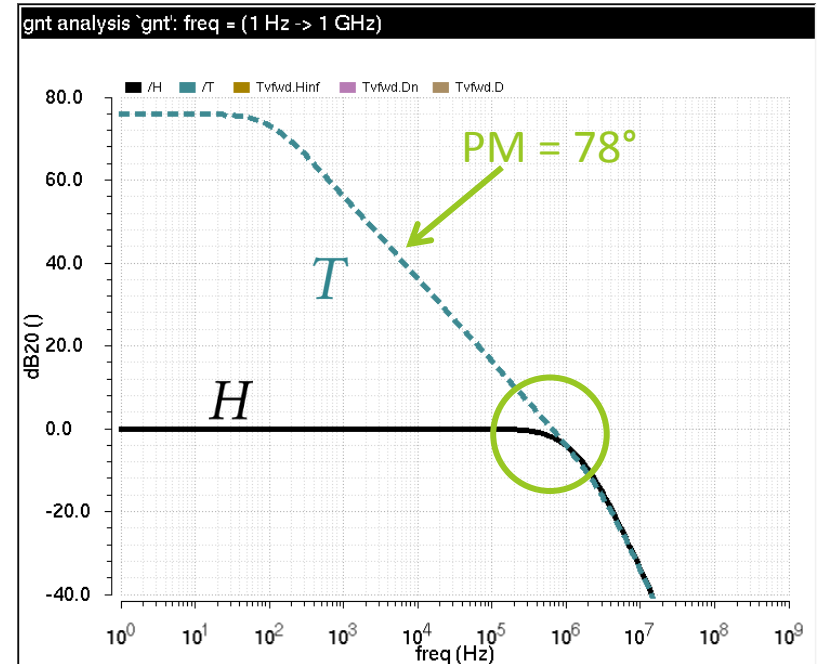
$$H' = H'_\infty \frac{1 + \frac{1}{T'_n}}{1 + \frac{1}{T'}}$$



Application example: reducing peaking, EET analysis nested in GFT analysis - results


Problem

Forward voltage loop gain
insufficient PM
↳ H shows peaking



$$T_{v,\text{fwd}} = H'$$
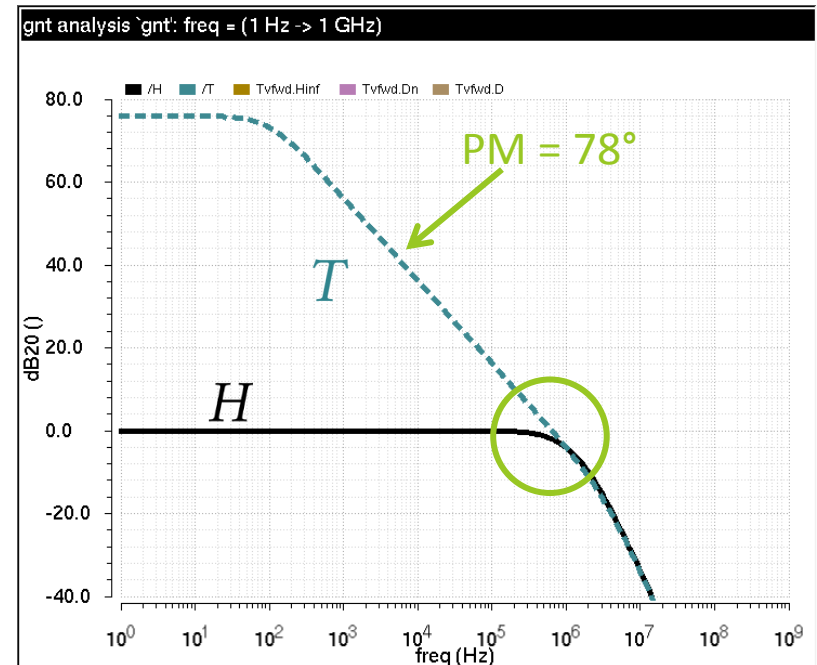
$$H' = H'_\infty \frac{1 + \frac{1}{T'_n}}{1 + \frac{1}{T'}}$$



Conclusion

GNT analysis integrated in ADE and ADE XL

Allows direct application of theorem

Valuable to increase insight, provides design guidance

Helpful instrument for design and analysis of electronic circuits and education of future designers

analogdesign.be

jochen.verbrugghe@intec.ugent.be
bart.moeneclaey@intec.ugent.be

References and acknowledgement

- R. D. Middlebrook, "The general feedback theorem: A final solution for feedback systems," IEEE Microwave Magazine, vol. 7, no. 2, pp. 50+, April 2006
- V. Vorperian, Fast analytical techniques for electrical and electronic circuits. 2002
- R. D. Middlebrook, "The DT and the CT: The Dissection Theorem and the Chain Theorem." [Online]. Available: <http://www.rdmiddlebrook.com/D-OA-Rules&Tools/index.asp>
- R. D. Middlebrook, "Null double injection and the extra element theorem," IEEE Transactions on education, vol. 32, no. 3, pp. 167-180, August 1989
- R. D. Middlebrook, V. Vorperian, and J. Lindal, "The N Extra Element Theorem," IEEE Trans. Circuits Syst. I Fundam. Theory Appl., vol. 45, no. 9, pp. 919–935, 1998
- J. Verbrugghe, B. Moeneclaey, "Implementation of the Dissection Theorem in Cadence Virtuoso", International Conference on Synthesis, Modeling, Analysis and Simulation Methods and Applications to Circuit Design, pp. 145-148, September, 2012
- M. Tian, V. Visvanathan, J. Hantgan, and K. Kundert, "Striving for small-signal stability," IEEE Circuits & Devices, vol. 17, no. 1, pp. 31-41, January 2001
- F. Wiedmann. Loop gain simulation. [Online]. Available: <http://sites.google.com/site/frankwiedmann/loopgain>

Research funded by a Ph.D. grant of the Agency for Innovation by Science and Technology of Flanders (IWT).